

## Linear Voltage Fan Speed Control Using Microchip's TC64X Family


Author: Microchip Technology Inc.

### INTRODUCTION

Pulse Width Modulation (PWM) fan speed control methodology pulse-width modulates a fan's full-rated power supply voltage at a low frequency, typically 30 Hz. A typical PWM circuit, consisting of a transistor in series with a fan, can be small and inexpensive because it is either fully on or completely off. This efficient control methodology affords a very wide speed-control range (typically 10% to 100% of full speed) because the fan motor is exposed to its full-rated voltage during the active portion of the PWM cycle.

PWM control works with standard, two-wire Brushless DC (BDC) fans of various sizes. However, very large fans (with operating currents of 0.5A or more) can sometimes produce an unwanted acoustic noise component when operated with PWM control. In most cases, this is remedied by slowing the edges of the output switching transistor with the addition of a small capacitor. In the most severe cases, this may not be sufficient, which forces the user to consider linear voltage speed control.

Linear voltage speed control operates by continuously varying the DC supply across the fan. The lower the voltage, the slower the fan operates. While this methodology eliminates the acoustic noise issue described earlier, it creates other problems. For example, the output device must be operated as a linear amplifier (instead of a switch), so its size and cost must be increased and may require heatsink mounting. Also, most fans cannot be operated at less than half the full-rated supply voltage, thereby limiting the fan speed control range to only 50% to 100% of maximum. With the inherent limitations of linear voltage speed control in mind, this application note describes a low-cost technique for operating the TC642/646/648 PWM Fan Managers in linear voltage speed control mode.

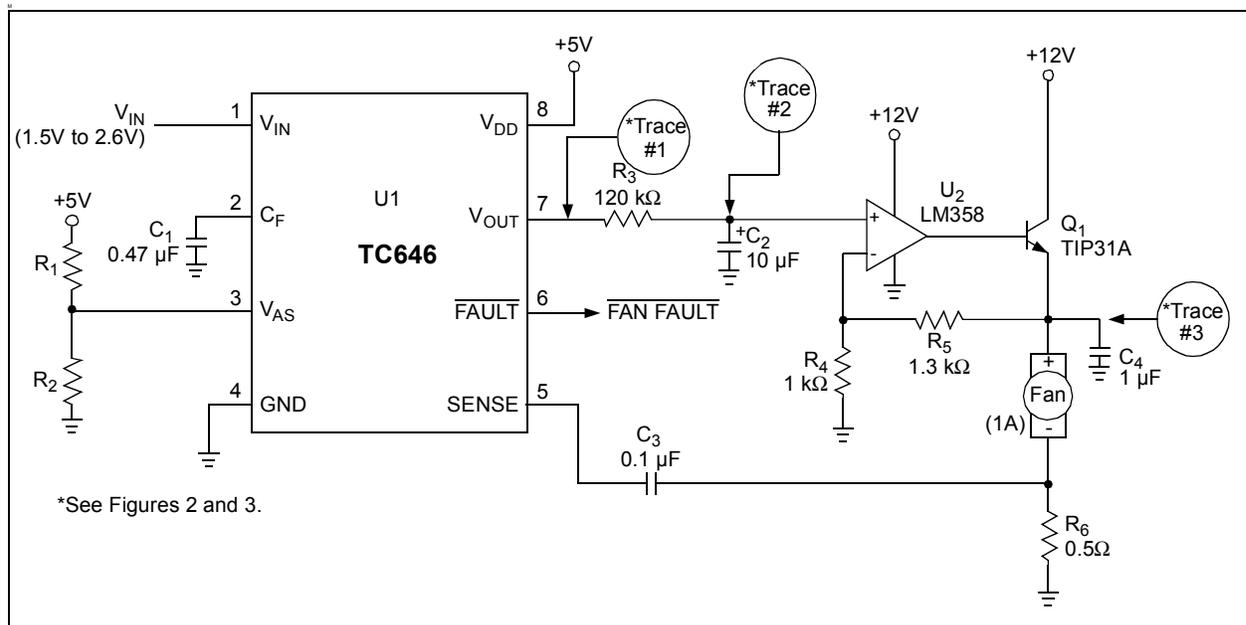

**FIGURE 1:** Linear Voltage Speed Control Circuit.

## MICROCHIP'S TC64X FAN MANAGERS


The TC642/646/648 Fan Managers are stand-alone, PWM output fan speed controllers/monitors that operate with any standard two-wire BDC fan. They control fan speed using a low frequency PWM, modulated by a 1.25V to 2.65V typical input signal. This is usually provided by a thermistor or other low-cost temperature sensor. The TC642 and TC646 have built-in fan fault detection circuits that monitor the fan current waveform for commutation pulses. On-board circuitry compares the presence (or absence) of these pulses to the fan's operating state to determine if a fault condition is present. For more information, please consult the TC642 (DS21444), TC646 (DS21446) and TC648 (DS21448) datasheets.

## LINEAR VOLTAGE SPEED CONTROL CIRCUIT


Figure 1 shows the circuit implementation for a linear voltage speed control/fan fault detector using the TC646 fan manager with auto-shutdown. All the features of the TC646 (including fan fault detection) remain intact. Compared to the TC646 circuit recommended in the datasheet, the circuit of Figure 1 adds a low-cost, single-supply Operational Amplifier (Op Amp) (such as an LM358), gain-setting resistors  $R_4$  and  $R_5$  and a PWM averaging circuit consisting of  $R_3$  and  $C_2$ . As is the case with all linear voltage fan speed control schemes, series-pass transistor  $Q_1$  must have sufficient power and current-handling capability to support the fan of choice. Depending on the voltage and current of this fan,  $Q_1$  may require a heatsink. The remaining circuitry components (i.e., values of  $R_1$ ,  $R_2$ ,  $R_6$ , and  $C_3$ ) are consistent with the recommended circuit configuration in the TC646 datasheet (DS21446).

The PWM output waveform from the TC646 is averaged by  $R_3$  and  $C_2$ . The averaged PWM signal is applied to a simple, non-inverting voltage amplifier consisting of Op Amp  $U_2$  and resistors  $R_4$  and  $R_5$ . Transistor  $Q_1$ , biased by the feedback loop around  $U_2$ , provides the output current necessary to drive the fan. As shown in Figure 2, the PWM signal (trace 1) is averaged (trace 2), resulting in the DC drive level applied to the fan (trace 3). Notice the PWM duty cycle in Figure 2 is 50.2%, resulting in a fan drive voltage of 6.1V (fan running at approximately half-speed). Figure 3 shows the effects of increasing PWM duty cycle to approximately 75%, causing a corresponding increase of the fan drive voltage to 8.7V.

The circuit configuration and values shown in Figure 1 will support 12V fans to a maximum operating current of 2A, (with the  $Q_1$  mounted on the appropriate heat-sink). Higher voltage and/or higher current fans can be supported using the appropriate operational amplifier/transistor combination.

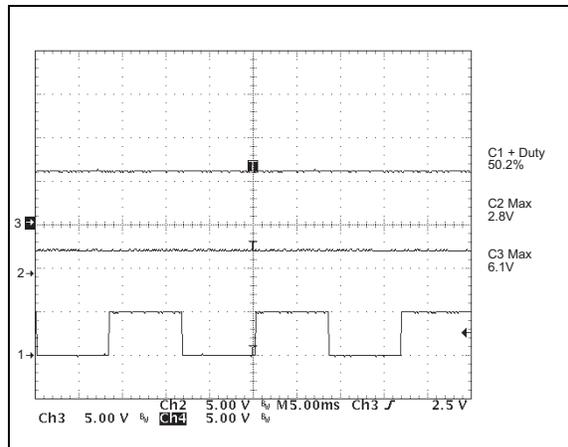

**FIGURE 2:** Waveform at 50% Duty Cycle.

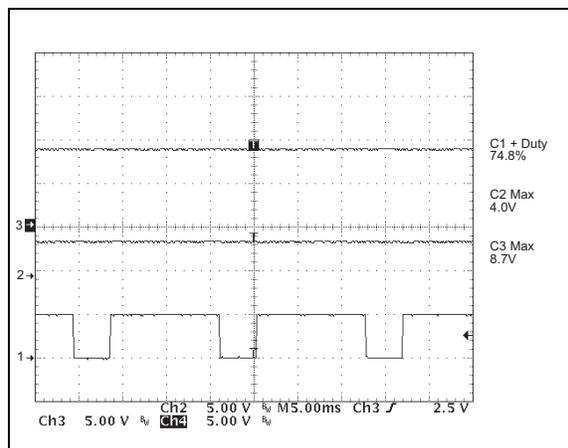

**FIGURE 3:** Waveform at 75% Duty Cycle.

## SUMMARY

The TC64X family of BDC Fan Managers can be operated in a linear voltage speed control mode with the addition of a few inexpensive components. In some cases, this speed control methodology is recommended for large fans and limits acoustic noise that would otherwise result from PWM speed control.

---

**Note the following details of the code protection feature on Microchip devices:**

- Microchip products meet the specification contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is one of the most secure families of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the Microchip products in a manner outside the operating specifications contained in Microchip's Data Sheets. Most likely, the person doing so is engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as "unbreakable."

Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our products. Attempts to break microchip's code protection feature may be a violation of the Digital Millennium Copyright Act. If such acts allow unauthorized access to your software or other copyrighted work, you may have a right to sue for relief under that Act.

---

Information contained in this publication regarding device applications and the like is intended through suggestion only and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. No representation or warranty is given and no liability is assumed by Microchip Technology Incorporated with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Use of Microchip's products as critical components in life support systems is not authorized except with express written approval by Microchip. No licenses are conveyed, implicitly or otherwise, under any intellectual property rights.

**Trademarks**

The Microchip name and logo, the Microchip logo, KEELoQ, MPLAB, PIC, PICmicro, PICSTART, PRO MATE and PowerSmart are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

FilterLab, microID, MXDEV, MXLAB, PICMASTER, SEEVAL and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Accuron, dsPIC, dsPICDEM.net, ECONOMONITOR, FanSense, FlexROM, fuzzyLAB, In-Circuit Serial Programming, ICSP, ICEPIC, microPort, Migratable Memory, MPASM, MPLIB, MPLINK, MPSIM, PICC, PICKit, PICDEM, PICDEM.net, PowerCal, PowerInfo, PowerTool, rPIC, Select Mode, SmartSensor, SmartShunt, SmartTel and Total Endurance are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

Serialized Quick Turn Programming (SQTP) is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.

© 2003, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

 Printed on recycled paper.



*Microchip received QS-9000 quality system certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona in July 1999 and Mountain View, California in March 2002. The Company's quality system processes and procedures are QS-9000 compliant for its PICmicro® 8-bit MCUs, KEELoQ® code hopping devices, Serial EEPROMs, microperipherals, non-volatile memory and analog products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001 certified.*



# MICROCHIP

## WORLDWIDE SALES AND SERVICE

### AMERICAS

#### Corporate Office

2355 West Chandler Blvd.  
Chandler, AZ 85224-6199  
Tel: 480-792-7200 Fax: 480-792-7277  
Technical Support: 480-792-7627  
Web Address: <http://www.microchip.com>

#### Rocky Mountain

2355 West Chandler Blvd.  
Chandler, AZ 85224-6199  
Tel: 480-792-7966 Fax: 480-792-4338

#### Atlanta

3780 Mansell Road, Suite 130  
Alpharetta, GA 30022  
Tel: 770-640-0034 Fax: 770-640-0307

#### Boston

2 Lan Drive, Suite 120  
Westford, MA 01886  
Tel: 978-692-3848 Fax: 978-692-3821

#### Chicago

333 Pierce Road, Suite 180  
Itasca, IL 60143  
Tel: 630-285-0071 Fax: 630-285-0075

#### Dallas

4570 Westgrove Drive, Suite 160  
Addison, TX 75001  
Tel: 972-818-7423 Fax: 972-818-2924

#### Detroit

Tri-Atria Office Building  
32255 Northwestern Highway, Suite 190  
Farmington Hills, MI 48334  
Tel: 248-538-2250 Fax: 248-538-2260

#### Kokomo

2767 S. Albright Road  
Kokomo, Indiana 46902  
Tel: 765-864-8360 Fax: 765-864-8387

#### Los Angeles

18201 Von Karman, Suite 1090  
Irvine, CA 92612  
Tel: 949-263-1888 Fax: 949-263-1338

#### San Jose

Microchip Technology Inc.  
2107 North First Street, Suite 590  
San Jose, CA 95131  
Tel: 408-436-7950 Fax: 408-436-7955

#### Toronto

6285 Northam Drive, Suite 108  
Mississauga, Ontario L4V 1X5, Canada  
Tel: 905-673-0699 Fax: 905-673-6509

### ASIA/PACIFIC

#### Australia

Microchip Technology Australia Pty Ltd  
Suite 22, 41 Rawson Street  
Epping 2121, NSW  
Australia  
Tel: 61-2-9868-6733 Fax: 61-2-9868-6755

#### China - Beijing

Microchip Technology Consulting (Shanghai)  
Co., Ltd., Beijing Liaison Office  
Unit 915  
Bei Hai Wan Tai Bldg.  
No. 6 Chaoyangmen Beidajie  
Beijing, 100027, No. China  
Tel: 86-10-85282100 Fax: 86-10-85282104

#### China - Chengdu

Microchip Technology Consulting (Shanghai)  
Co., Ltd., Chengdu Liaison Office  
Rm. 2401-2402, 24th Floor,  
Ming Xing Financial Tower  
No. 88 TIDU Street  
Chengdu 610016, China  
Tel: 86-28-86766200 Fax: 86-28-86766599

#### China - Fuzhou

Microchip Technology Consulting (Shanghai)  
Co., Ltd., Fuzhou Liaison Office  
Unit 28F, World Trade Plaza  
No. 71 Wusi Road  
Fuzhou 350001, China  
Tel: 86-591-7503506 Fax: 86-591-7503521

#### China - Hong Kong SAR

Microchip Technology Hongkong Ltd.  
Unit 901-6, Tower 2, Metroplaza  
223 Hing Fong Road  
Kwai Fong, N.T., Hong Kong  
Tel: 852-2401-1200 Fax: 852-2401-3431

#### China - Shanghai

Microchip Technology Consulting (Shanghai)  
Co., Ltd.  
Room 701, Bldg. B  
Far East International Plaza  
No. 317 Xian Xia Road  
Shanghai, 200051  
Tel: 86-21-6275-5700 Fax: 86-21-6275-5060

#### China - Shenzhen

Microchip Technology Consulting (Shanghai)  
Co., Ltd., Shenzhen Liaison Office  
Rm. 1812, 18/F, Building A, United Plaza  
No. 5022 Binhe Road, Futian District  
Shenzhen 518033, China  
Tel: 86-755-82901380 Fax: 86-755-82966626

#### China - Qingdao

Rm. B503, Fullhope Plaza,  
No. 12 Hong Kong Central Rd.  
Qingdao 266071, China  
Tel: 86-532-5027355 Fax: 86-532-5027205

#### India

Microchip Technology Inc.  
India Liaison Office  
Divyasree Chambers  
1 Floor, Wing A (A3/A4)  
No. 11, O'Shaughnessey Road  
Bangalore, 560 025, India  
Tel: 91-80-2290061 Fax: 91-80-2290062

### Japan

Microchip Technology Japan K.K.  
Benex S-1 6F  
3-18-20, Shinyokohama  
Kohoku-Ku, Yokohama-shi  
Kanagawa, 222-0033, Japan  
Tel: 81-45-471-6166 Fax: 81-45-471-6122

### Korea

Microchip Technology Korea  
168-1, Youngbo Bldg. 3 Floor  
Samsung-Dong, Kangnam-Ku  
Seoul, Korea 135-882  
Tel: 82-2-554-7200 Fax: 82-2-558-5934

### Singapore

Microchip Technology Singapore Pte Ltd.  
200 Middle Road  
#07-02 Prime Centre  
Singapore, 188980  
Tel: 65-6334-8870 Fax: 65-6334-8850

### Taiwan

Microchip Technology (Barbados) Inc.,  
Taiwan Branch  
11F-3, No. 207  
Tung Hua North Road  
Taipei, 105, Taiwan  
Tel: 886-2-2717-7175 Fax: 886-2-2545-0139

### EUROPE

#### Austria

Microchip Technology Austria GmbH  
Durisolstrasse 2  
A-4600 Wels  
Austria  
Tel: 43-7242-2244-399  
Fax: 43-7242-2244-393

#### Denmark

Microchip Technology Nordic ApS  
Regus Business Centre  
Lautrup høj 1-3  
Ballerup DK-2750 Denmark  
Tel: 45 4420 9895 Fax: 45 4420 9910

#### France

Microchip Technology SARL  
Parc d'Activite du Moulin de Massy  
43 Rue du Saule Trapu  
Batiment A - 1er Etage  
91300 Massy, France  
Tel: 33-1-69-53-63-20 Fax: 33-1-69-30-90-79

#### Germany

Microchip Technology GmbH  
Steinheilstrasse 10  
D-85737 Ismaning, Germany  
Tel: 49-89-627-144 0 Fax: 49-89-627-144-44

#### Italy

Microchip Technology SRL  
Centro Direzionale Colleoni  
Palazzo Taurus 1 V. Le Colleoni 1  
20041 Agrate Brianza  
Milan, Italy  
Tel: 39-039-65791-1 Fax: 39-039-6899883

#### United Kingdom

Microchip Ltd.  
505 Eskdale Road  
Winkersley Triangle  
Wokingham  
Berkshire, England RG41 5TU  
Tel: 44 118 921 5869 Fax: 44-118 921-5820

12/05/02